

Serial Adder :-

- the parallel adder performs the addition of two binary number at a relatively faster rate.
- the disadvantage of the parallel adder is that it requires a relatively large amount of logic circuitry.
- this increases in direct proportion with the no. of bits in the numbers being added.
- In serial addition, the addition operation is carried out bit-by-bit. therefore, the serial adder requires simpler circuitry than a parallel adder but results in a low speed of operation.

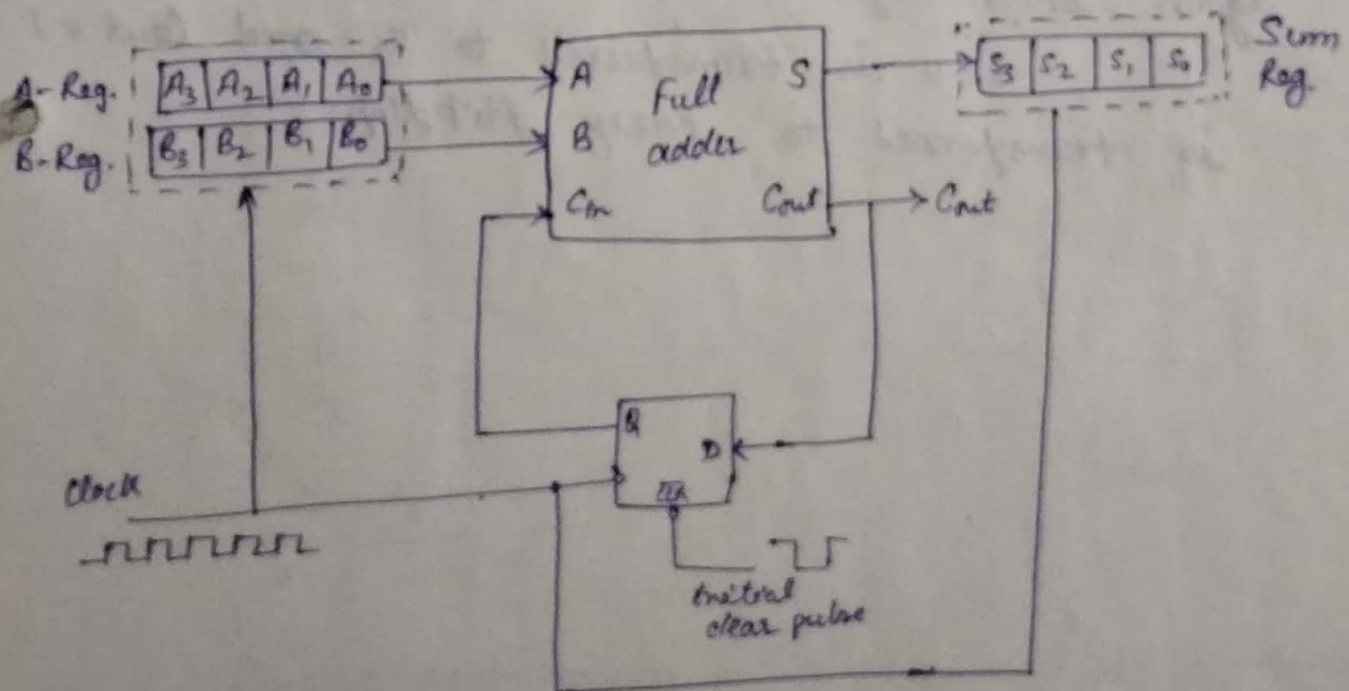


Fig:- 4-bit Serial Adder

Operation :-

$$A_3 A_2 A_1 A_0 = 0111$$

$$B_3 B_2 B_1 B_0 = 0010$$

$$\begin{array}{r} 1001 \rightarrow \text{Result} \end{array}$$

Before clock :-

$$A_0 = 1$$

$$B_0 = 0$$

$$C_{in} = 0, \text{ then } S = 1 \text{ \& } C_{out} = 0$$

1st clock :- value in shift Reg. A & B shift one bit from left to right.

- Sum (S) is transferred to S_3 of Sum Reg.
- Cout is transferred to the carry flip flop.

2nd clock :-

Now

$$A_0 = 1$$

$$B_0 = 1$$


$$C_{in} = 0$$

} at full adder i/p.

$$\text{so } S = 0 \text{ \& } C_{out} = 1$$


when 2nd clock pulse occurs, A, B & Sum registers again shift right;

 $S = 0$ is transferred to S_3 and $C_{out} = 1$ is transferred to carry flip flop.



Parallel Adder :

 → Two or more full adders are connected to form Binary parallel adder.



For 4 bit


3FA and 1 HA required
(or)
4 FA
or
7 HA and 3 OR gate.

→ Parallel adder is used to add group of bits. In this to add two n bits numbers, it requires-

$(n-1)$ FA and 1 HA
(or)
 n FA
(or)
 $(2n-1)$ HA and $(n-1)$ OR gates

4 Bit Parallel adder :- (carry propagate adder)


→ Also called Ripple carry adder.

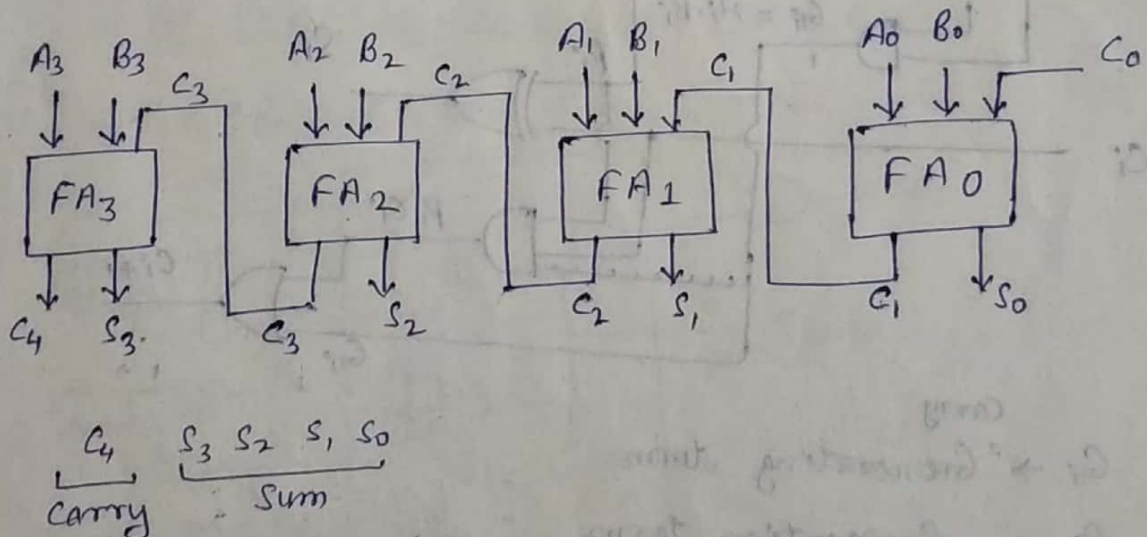

→ In Parallel adder shown in fig. each full adder will provide Two logic gate delays.

→ In 4-bit Parallel adder to provide final result it requires 8-logic gate delays. ($8 \times t_{pd}$)


n- Bit Parallel adder -

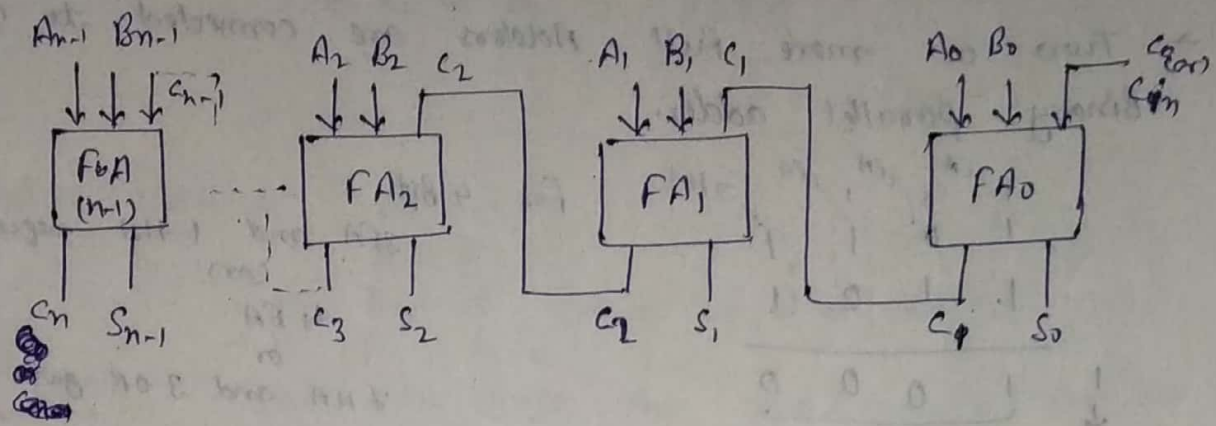

→ $n \times 2$ tpd delay will provide result.

Look Ahead Carry Generator, (or Carry Look Ahead Adder)

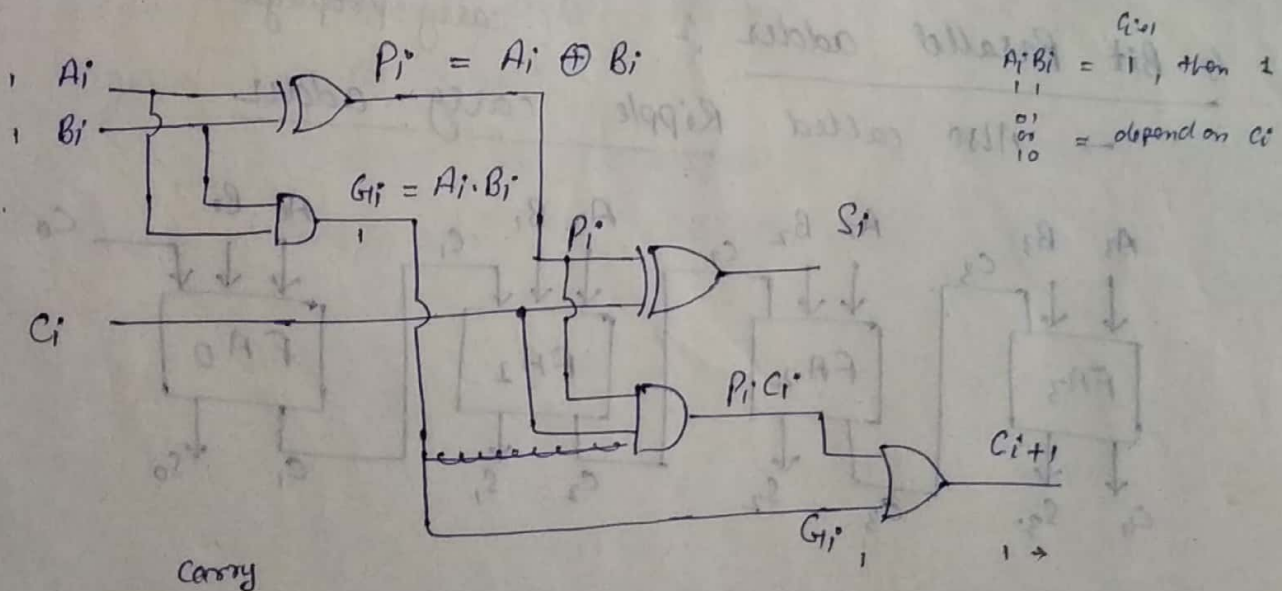→ This is the addition technique which eliminates the problem due to interstage carry delay. The look ahead carry addition will therefore speedup the addition process.



$G_i \rightarrow$ Generating term

$P_i \rightarrow$ Propagation term

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

$$S_i = P_i \oplus C_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = P_i C_i + G_i = (A_i \oplus B_i) C_i + A_i B_i$$

4 Bit look ahead carry adder :-

(23)

$P_0 = A_0 \oplus B_0$	$G_0 = A_0 B_0$	$S_0 = P_0 \oplus C_0$
$P_1 = A_1 \oplus B_1$	$G_1 = A_1 B_1$	$S_1 = P_1 \oplus C_1$
$P_2 = A_2 \oplus B_2$	$G_2 = A_2 B_2$	$S_2 = P_2 \oplus C_2$
$P_3 = A_3 \oplus B_3$	$G_3 = A_3 B_3$	$S_3 = P_3 \oplus C_3$

$$C_{i+1} = P_i C_i + G_i$$

$i=0$

$$C_1 = C_{0+1} = P_0 C_0 + G_0$$

$i=1$

$$C_2 = C_{1+1} = P_1 C_1 + G_1$$

$$= P_1 [P_0 C_0 + G_0] + G_1$$

$$= P_1 P_0 C_0 + P_1 G_0 + G_1$$

$i=2$

$$C_3 = C_{2+1} = P_2 C_2 + G_2$$

$$= P_2 [P_1 P_0 C_0 + P_1 G_0 + G_1] + G_2$$


$$= P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

$i=3$

$$C_4 = C_{3+1} = P_3 C_3 + G_3$$

$$= P_3 [P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2] + G_3$$
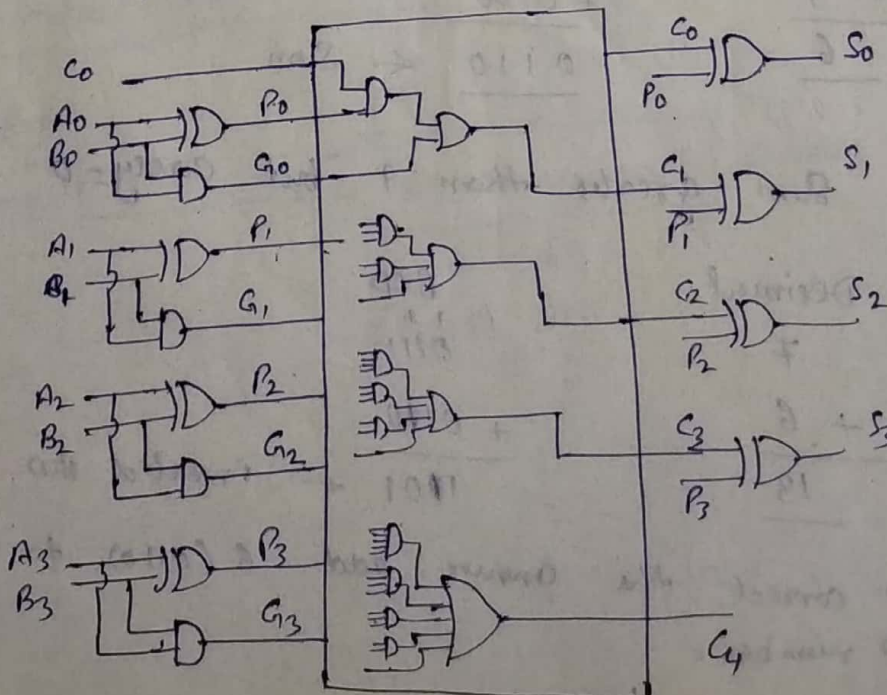
$$= P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$



→ No. of AND gate and OR gate

$$= 1 + 2 + 3 + 4 = 10 \text{ AND}$$

$$\rightarrow = 4 \text{ (OR)}$$

AND gate = $\sum_{i=1}^n i$

OR gate = n

- carry ckt is implemented using Two level AND-OR gates
- To generate carry o/p it requires 3 logic gate delays
- To generate sum o/p 4 logic gates delay required.
- Fastest adder Because it is independent of previous stage.
- Disadvantage → Complexity will increase as the no. of bits increase.

Introduction to BCD adder -

Case-I - Sum equal to or less than 9 but carry = 0.

Decimal	BCD
2	0010
+ 4	+ 0100
6	0110 ← Sum

Case-II - Sum greater than 9 but carry = 0

Decimal	BCD
7	0111
+ 6	+ 0100
13	1001 ← invalid BCD

- To correct the answer add 6 (0110) to the invalid BCD number.

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 0001\ 0011 \\ \hline 1\quad\quad 3 \end{array} \leftarrow \text{valid BCD Number}$$


Case-(iii) - Sum less than or equal to 9 but carry = 1.


Decimal	BCD
9	1001
+ 7	+ 0111
<u>16</u>	<u>10000</u>

← wrong result.
Carry sum is invalid.

$$\begin{array}{r} 00010000 \\ + 0110 \\ \hline 00010110 \\ \hline 1\quad\quad 6 \end{array} \leftarrow \text{valid BCD No.}$$

Block diagram of BCD adder

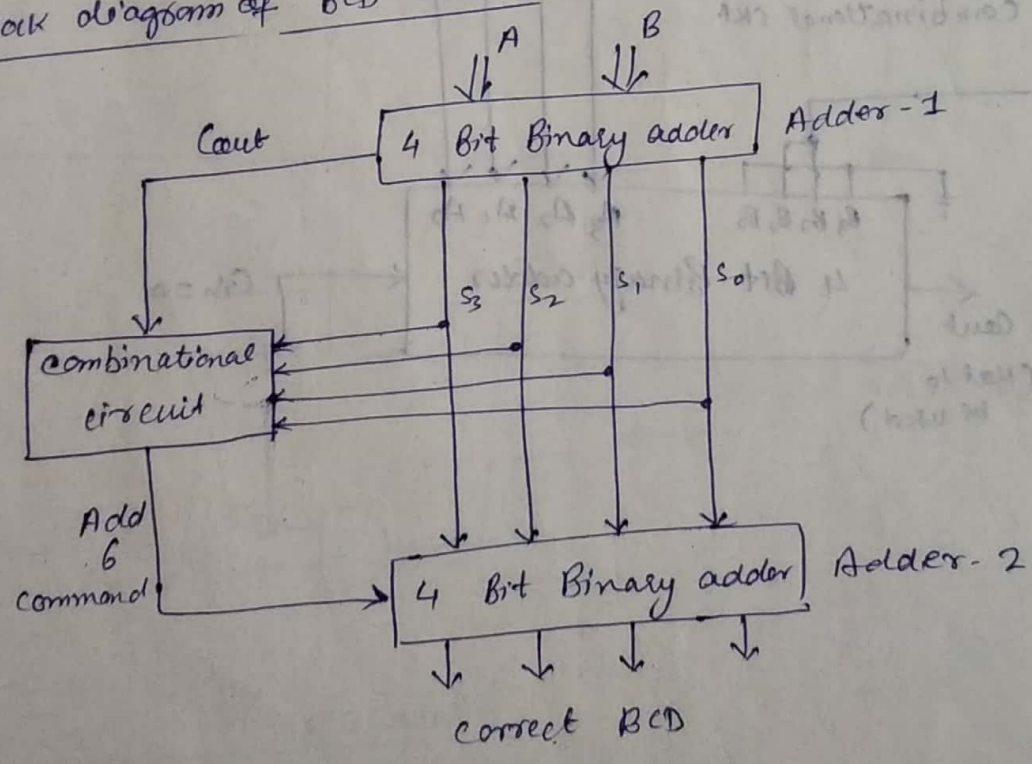

 

$$Y = S_3S_2 + S_3S_1$$

